

3-2022

## Experiment 2.08: Series RLC ac-Circuit

Diego Castano

Victor Castro

Follow this and additional works at: [https://nsuworks.nova.edu/physics\\_labs](https://nsuworks.nova.edu/physics_labs)



Part of the [Physics Commons](#)

This Book has supplementary content. View the full record on NSUWorks here:

---

## I. EXPERIMENT 2.08: SERIES RLC AC-CIRCUIT

### A. Abstract

A coil with unknown inductance and internal resistance is connected in series with a known capacitance in an ac-circuit. The current in the circuit is monitored as the driving frequency is varied. The maximum current is obtained at resonance.

### B. Formulas

$$\Delta V_S = IZ(f_0) = I_0R \quad (1)$$

$$4\pi^2 f_0^2 = \frac{1}{LC} \quad (2)$$

where these equations are relevant to a series RLC ac-circuit with capacitor (of known capacitance  $C$ ) and a coil with internal resistance  $R$  and inductance  $L$  and where  $f_0$  is the resonant frequency.

### C. Description and Background

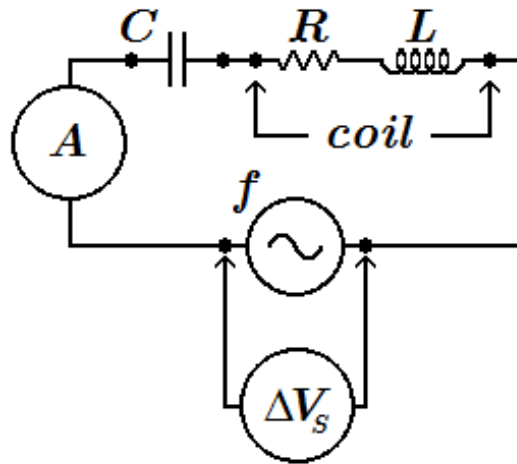


FIG. 1. RLC circuit set-up for the experiment.

The rms current in an LRC series circuit (Fig. 1) is given by

$$I = \frac{\Delta V_S}{Z} = \frac{\Delta V_S}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \quad (3)$$

where  $\omega = 2\pi f$  is the angular frequency of the ac source. Because the reactance of inductors and capacitors depends on  $f$ , the current in an LRC circuit also depends on frequency. A graph of  $I$  versus  $f$  is shown in Fig. 2 for particular values of  $R$ ,  $L$ , and  $C$ . For smaller values of resistance, the resonance peak will be higher and sharper.

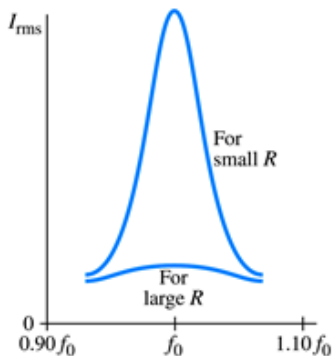


FIG. 2.  $I$  versus  $f$ .

From Eq. (3) we see that the current will be maximum at an angular frequency,  $f_0$ , that satisfies Eq. (2). Thus, when the source frequency matches  $f_0$  the circuit is said to be in resonance, and  $f_0$  is called the resonant frequency. At this frequency, the impedance is purely resistive,  $Z = R$ . And so, from Eq. (3), the voltage from the source would be given by Eq. (1).

#### D. Procedure

1. Set up the circuit in the figure on the next page.
2. Make sure the ammeter is set to measure ac current in the milli-Amp range. Turn on the sine wave generator and adjust the starting frequency to  $f = 40 \text{ Hz}$ . Set the voltage to  $\Delta V_S = 5 \text{ Volts}$ . and record the resulting current.
3. Repeat this procedure for increasing frequencies as tabulated below.

### E. Measurements

$\Delta V_S$ [ <i>Volts</i> ]	
rated capacitance, $C$ [ $\mu F$ ]	

$f$ [ <i>Hz</i> ]	$I$ [ <i>mA</i> ]
40	
45	
50	
55	
60	
65	
70	
75	
80	
85	
90	
95	
100	

## F. Instructions

1. Use the excel file, **RLCPlot.xlsx**, to plot  $I$  vs.  $f$ , and determine the resonant frequency,  $f_0$ , and current,  $I_0$ , from the graph.
2. Use Eqs. (1) and (2) to determine the internal resistance,  $R$ , and inductance,  $L$ , of the coil.
3. Submit your  $I$  vs.  $f$  graph.

### G. Calculations

resonant frequency, $f_0$ [ $Hz$ ]	
resonant current, $I_0$ [ $mA$ ]	
internal coil resistance, $R$ [ $\Omega$ ]	
internal coil inductance, $L$ [ $mH$ ]	